

4. Connecting the Solenoid Lock

- **Power the Solenoid Lock:**
 - Connect the positive terminal of the solenoid lock to the NO (Normally Open) terminal of the relay.
 - Connect the common (COM) terminal of the relay to the positive terminal of your 12V power supply.
 - Connect the negative terminal of the solenoid lock to the negative terminal of your 12V power supply.
- **Power Supply:** Ensure the 12V power supply is correctly connected to the solenoid lock using a DC barrel jack adapter if necessary.

5. Powering the Raspberry Pi

- Use the Raspberry Pi's dedicated power supply (5V) and ensure it's not powered from the same 12V supply as the solenoid lock.

Summary of Connections:

1. **Camera Module:** Connected to the CSI port on the Raspberry Pi.
2. **Relay Module:**
 - VCC to 5V on Raspberry Pi.
 - GND to GND on Raspberry Pi.
 - IN to GPIO 17 on Raspberry Pi.

Hardware Components and Connections

1. Components List

- Raspberry Pi 3 or 4
- Raspberry Pi Camera Module
- Relay Module
- Solenoid Lock (12V)
- 12V Power Supply
- DC Barrel Jack Adapter
- Jumper Wires

2. Connecting the Raspberry Pi Camera Module

- **Attach the Camera:** Connect the camera module to the Raspberry Pi's camera interface (CSI) slot.
- **Ensure Proper Alignment:** The blue side of the ribbon cable should face the Ethernet port, and the shiny contacts should face the HDMI port.

3. Relay Module Connection

- **Relay Pinout:** The relay module typically has three pins:
 - **VCC:** Connect to 5V on the Raspberry Pi.
 - **GND:** Connect to a ground (GND) pin on the Raspberry Pi.
 - **IN:** Connect to GPIO pin 17 on the Raspberry Pi (or another GPIO pin if preferred).